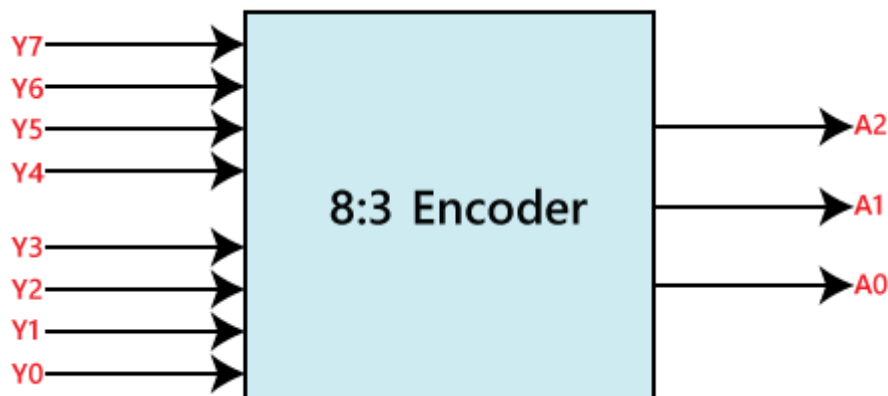


## ENCODERS:

An **Encoder** is a combinational circuit that performs the reverse operation of Decoder. It has maximum of  $2^n$  input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes  $2^n$  input lines with 'n' bits. It is optional to represent the enable signal in encoders...

The 8 to 3 line Encoder is also known as **Octal to Binary Encoder**. In 8 to 3 line encoder, there is a total of eight inputs, i.e.,  $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6$ , and  $Y_7$  and three outputs, i.e.,  $A_0, A_1$ , and  $A_2$ . In 8-input lines, one input-line is set to true at a time to get the respective binary code in the output side. Below are the block diagram and the truth table of the 8 to 3 line encoder.

### Block Diagram:



## RTL CODE:

```
module DeCoders(input [7:0]Y, output [2:0]A);  
    assign A[0]= Y[4] | Y[5] | Y[6] | Y[7];  
    assign A[1]= Y[2] | Y[3] | Y[6] | Y[7];  
    assign A[2]= Y[1] | Y[3] | Y[5] | Y[7];  
endmodule
```

## TESTBENCH:

```
module testbench;
    reg [7:0]Y;
    wire [2:0]A;
    int i;
    DeCoders a1 (Y,A);
    initial
        begin
            $dumpfile(".vcd");
            $dumpvars(1);
        end
    initial
        begin
            Y=8'b1;
            for(i=0;i<8;i++)
                begin
                    #10 Y=Y<<1;
                end
            end
        initial
            begin
                #60 $finish();
            end
    endmodule
```

