Day 25

BCD Seven Segment Decoder:

BCD to seven segment decoder has four input lines (A, B, C and D) and 7 output lines (a, b, c, d, e, f and g), this output is given to seven segment LED display which displays the decimal number depending upon inputs.


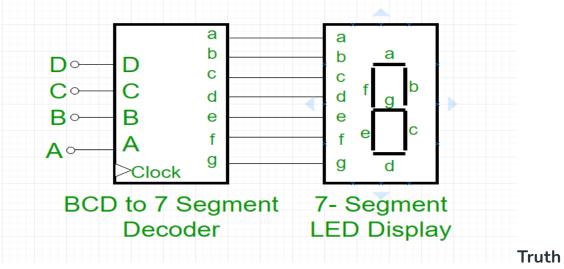


Table – For common cathode type BCD to seven segment decoder:

Α	В	С	D	а	b	С	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

• For Common Anode type seven segment LED display, we only have to interchange all '0s' and '1s' in the output side i.e., (for a, b, c, d, e, f, and g replace all '1' by '0' and vice versa) and solve using K-map.

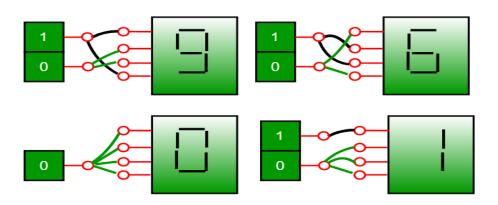- Output for first combination of inputs (A, B, C and D) in Truth Table corresponds to '0' and last combination corresponds to '9'. Similarly rest corresponds from 2 to 8 from top to bottom.
- BCD numbers only range from 0 to 9, thus rest inputs from 10-F are invalid inputs.



RTL CODE:

module BCDtoSevenSegment(input [3:0] bcd,output reg [6:0] seg);

```
always @ (bcd) begin
case (bcd)
4'b0000: seg = 7'b11111110;
4'b0001: seg = 7'b0110000;
4'b0010: seg = 7'b1101101;
4'b0101: seg = 7'b11110011;
4'b0101: seg = 7'b1011011;
4'b0110: seg = 7'b1011111;
```

```
4'b0111: seg = 7'b1110100;

4'b1000: seg = 7'b1111111;

4'b1001: seg = 7'b1110011;

default: seg = 7'b00000000;

endcase

end

endmodule
```

TESTBENCH:

```
module testbench;

reg [3:0]bcd;

wire [6:0]seg;

BCDtoSevenSegment a1( bcd, seg);

initial

begin

$dumpfile(".vcd");

$dumpvars(1);

end

initial

begin

bcd = 0;

#10 bcd =1;
```

```
#10 bcd =2;
#10 bcd =3;
#10 bcd =4;
#10 bcd =5;
#10 bcd =6;
#10 bcd =7;
#10 bcd =8;
#10 bcd =9;
end
initial
begin
#50 $finish();
end
endmodule
```

