 


FULL SUBTRACTOR

EXPLANATION:

The Half Subtractor is used to subtract only two numbers. To overcome this problem, a full subtractor was designed. The full subtractor is used to subtract three 1-bit numbers A, B, and C, which are minuend, subtrahend, and borrow, respectively. The full subtractor has three input states and two output states i.e., diff and borrow.



DIFF: $(A \text{ XOR } B) \text{ XOR } B_{in}$

BORROW OUT: $A'B_{in} + A'B + BB_{in}$

RTL CODE:

DATAFLOW METHOD:

```
module Full_subtractor(A,B,C,diff,brw);  
    input A,B,C;  
    output diff,brw;  
    assign diff=A^B^C;  
    assign brw=!A&B|(C&~(A^B));  
endmodule
```

BEHAVIOURAL METHOD:

```
module  
Full_subtractor(A  
,B,C,diff,brw);  
    input A,B,C;  
    output diff,brw;
```

```
always@(*);  
begin  
    diff=A^B^C;  
    brw=!A&B|(C&~(A^B));  
end  
endmodule
```


TEST BENCH:

```
module testbench;  
    reg A,B,C;  
    wire diff,brw;  
    integer i;  
    Full_subtractor a1(A,B,C,diff,brw);  
    initial  
        begin  
            $dumpfile("dump.vcd");  
            $dumpvars(1);  
        end  
    initial  
        begin  
            A=0;B=0;C=0;  
        end  
    initial  
        begin  
            for(i=1;i<8;i=i+1)  
                begin  
                    #10{A,B,C}=i;  
                end  
            end  
        end  
    initial  
        begin
```


```

        #60$finish();
    end
endmodule

```

 

FULLSUBTRACTOR USING HALF SUBTRACTOR

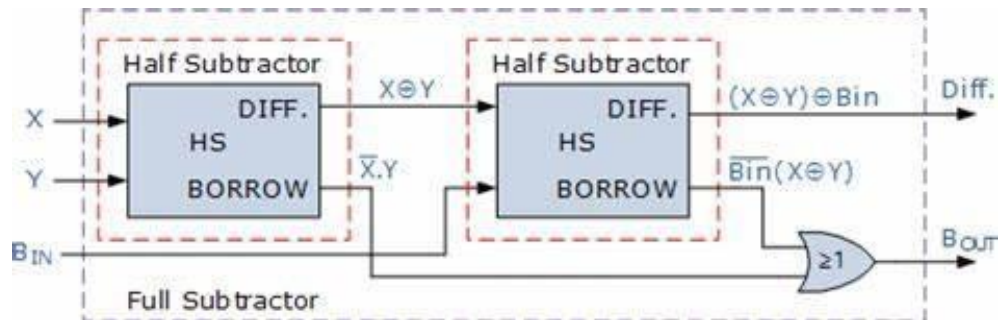

RTL CODE:

```

module full_subtractor(d,barr,a,b,c);

```

```

    input a,b,c; output d,barr;

```

```

    wire p, q, r; half_subtractor

```

```

    u4(p,q,a,b);

```

```

    half_subtractor u5(d,p,c);

```

```

    or_gate u6(barr, p,q);

```

```

endmodule TEST

```

BENCH:

```

module testbench;

```

```

    reg a,b,c;    wire d,barr;

```

```

    integer i;    full_sub

```

```
a1(d,barr,a,b,c);    initial
begin
    $dumpfile("dump.vcd");
$dumpvars(1);    end
initial    begin
a=0;b=0;c=0;    end    initial
begin    for(i=1;i<8;i=i+1)
begin
    #10 {a,b,c}=i;
end    end    initial
begin    #60
$finish();    end
endmodule
```