
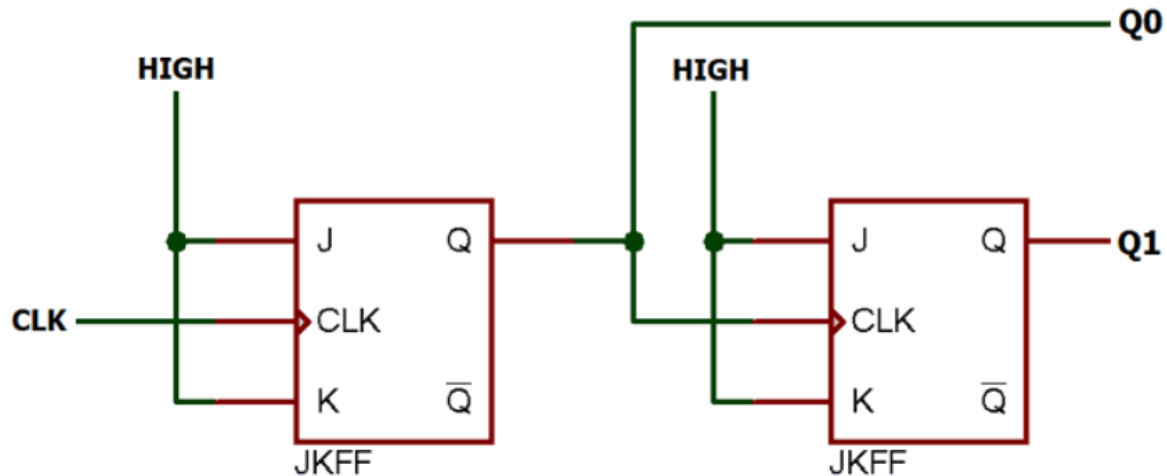


DAY 27

2 BIT ASYNCHRONOUS COUNTER:

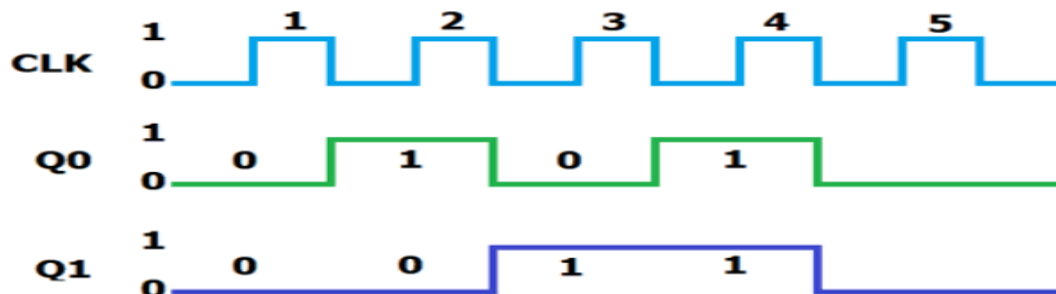

A 2-bit ripple counter is shown in the above figure. The external clock is connected to the clock input of the first flip-flop. So, this is why the first flip-flop changes the state at the quick falling edge of the clock pulse. But the second flip-flop changes only when it is triggered by the Q output of the first flip-flop. Due to an essential propagation delay in the circuit through a flip-flop, the change in the input clock pulse and change of the Q output of the first flip-flop can never occur at the same time giving the exact result. Therefore, the triggering of flip-flops cannot be simultaneous



Explanation

The transitions of Q 0, Q 1, and clock pulse in the figure of the timing diagram above are simultaneous. This phenomenon occurred here although it is an asynchronous counter. There is a small delay between the clock and the first and second transitions in the above counter.

All the clear inputs are connected together so that a single pulse can clear all the flip-flops before the counting of bits. The clock pulse given into the first flip-flop is rippled through the other counters after the propagation delay. Hence, its name is a ripple counter.

The above two-bit ripple counter has four states. There is the placement of each counter to correspond to the account value. Like the 2-bit counter, a counter having n number of flip-flops can have 2 to the power n states. These numbers of states are asserted as mod numbers. Thus, for a 2-bit counter, there is a mod 4 counter by the mechanism of 2 to the power n. Therefore, a bit counter can also be called a mod 4 counter

RTL CODE:

```
module jkff(input j,k,clk, output reg q,output reg qbar);
    always@(negedge clk)
    begin
        case({j,k})

            2'b00: q <=q;
            2'b01: q <=0;
            2'b10: q <=1;
            2'b11: q <= ~q;
```

```

        endcase
        assign qbar= ~q;
    end
endmodule

module Asynchronous_counter(input [1:0]j,input[1:0]k,clk,output
q,qbar,[1:0]count);
    wire QA,QB;
    jkff a1(j[0],k[0],clk,QA,QB);
    jkff a2(j[1],k[1],QA,q,qbar);
    assign count={q,QA};
endmodule

```

TEST BENCH:

```

module testbench;
    reg [1:0] j;
    reg [1:0] k;
    reg clk;
    wire q, qbar;
    wire [1:0]count;
    Asynchronous_counter s1(j, k, clk, q, qbar, count);

    initial begin
        $dumpfile("dump.vcd");

```

```

    $dumpvars(1);
end

initial begin
    clk = 0;
    forever #10 clk = ~clk;
end

```

```

initial begin
    repeat (5) begin

        j = $random;
        k = $random;

        #5 ;
    end
end


```

```

initial
    #60 $finish();

```

Endmodule

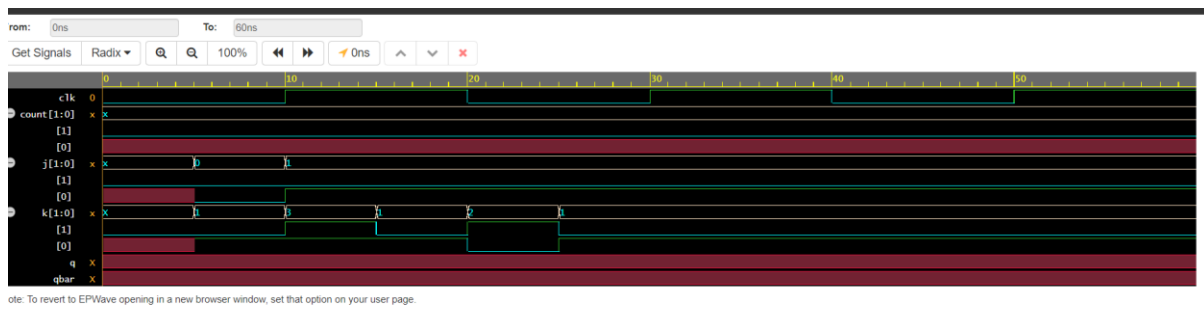

ote: To revert to EPWave opening in a new browser window, set that option on your user page.

