

2 BIT COMPARATOR:

A Comparator is a **combinational circuit** that gives output in terms of $A > B$, $A < B$, and $A = B$. This is entirely expected from the name. A digital comparator's purpose is to compare numbers and represent their relationship with each other.

A comparator used to compare two binary numbers each of two bits is called a 2-bit comparator. It consists of TWO inputs and three outputs to generate less than, equal to, and greater than between two



Figure No. 3: Block diagram of 2-Bit Comparator

RTL CODE:

```
module two_bit_comparator(input A, B,output G, e, L);
assign e = (A == B);
assign L = (A < B);
assign G = (A > B);
endmodule
```

TEST BENCH:

```
module testbench;
```

```

reg A,B;
wire G,e,L;
two_bit_comparator C1 (A,B,G,e,L);
initial
begin
    $dumpfile(".vcd");
    $dumpvars(1);
end
initial
begin
    A=0;B=0;
    #10 A=0;B=1;
    #10 A=1;B=0;
    #10 A=1;B=1;
end
initial
begin
    #50 $finish();
end
endmodule

```

